

Session 1



Power Supply Design

Aneesh Kumar

What the session is about?

- Why do we use Power Supply?
- What is Power Supply?
- Components
- SMPS

Question

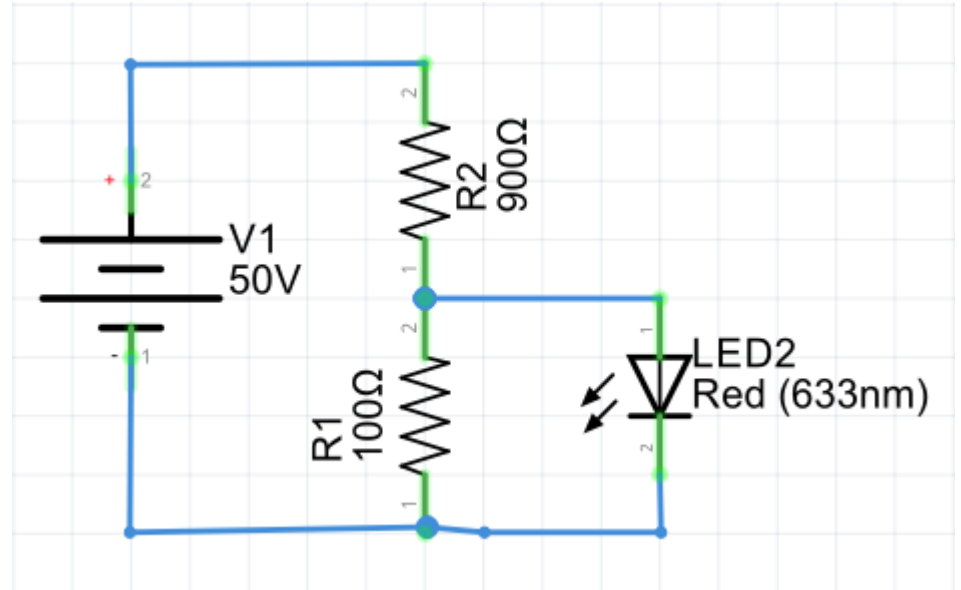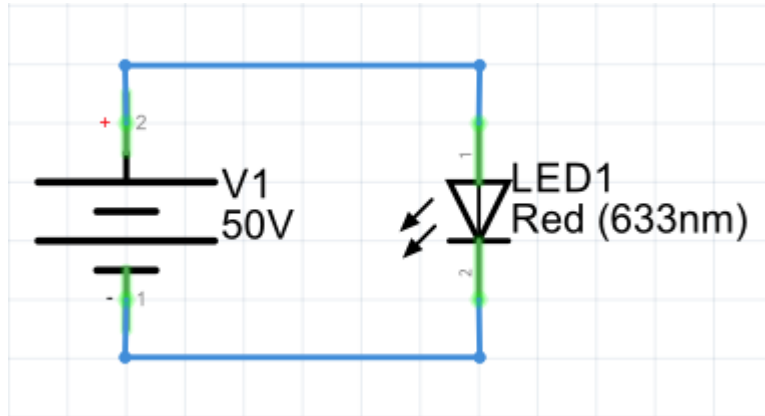


What is Power Supply?

- Power Supply supplies electrical energy to the electrical load(s). Typically these loads are integrated into other devices.
eg. Power Supply in computers.
- Converts one form of energy into other. e.g Solar Cells

Regulated DC Power Supply

- Steps-down the AC Supply
- Produces a varying DC Supply
- Filters out the variations
- Stable output.


Block Diagram

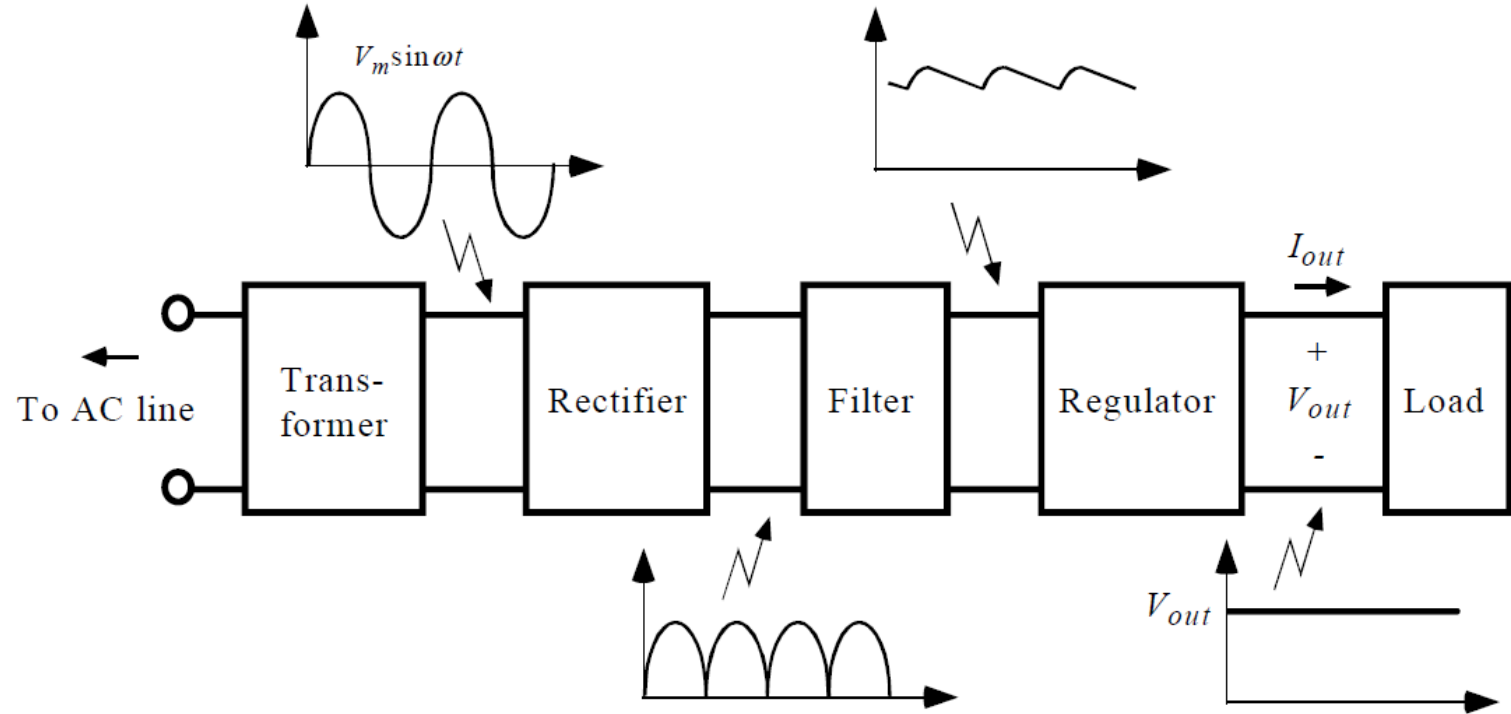


Components of a typical linear power supply

Source: <http://www.learnabout-electronics.org/PSU/psu10.php>

Circuit

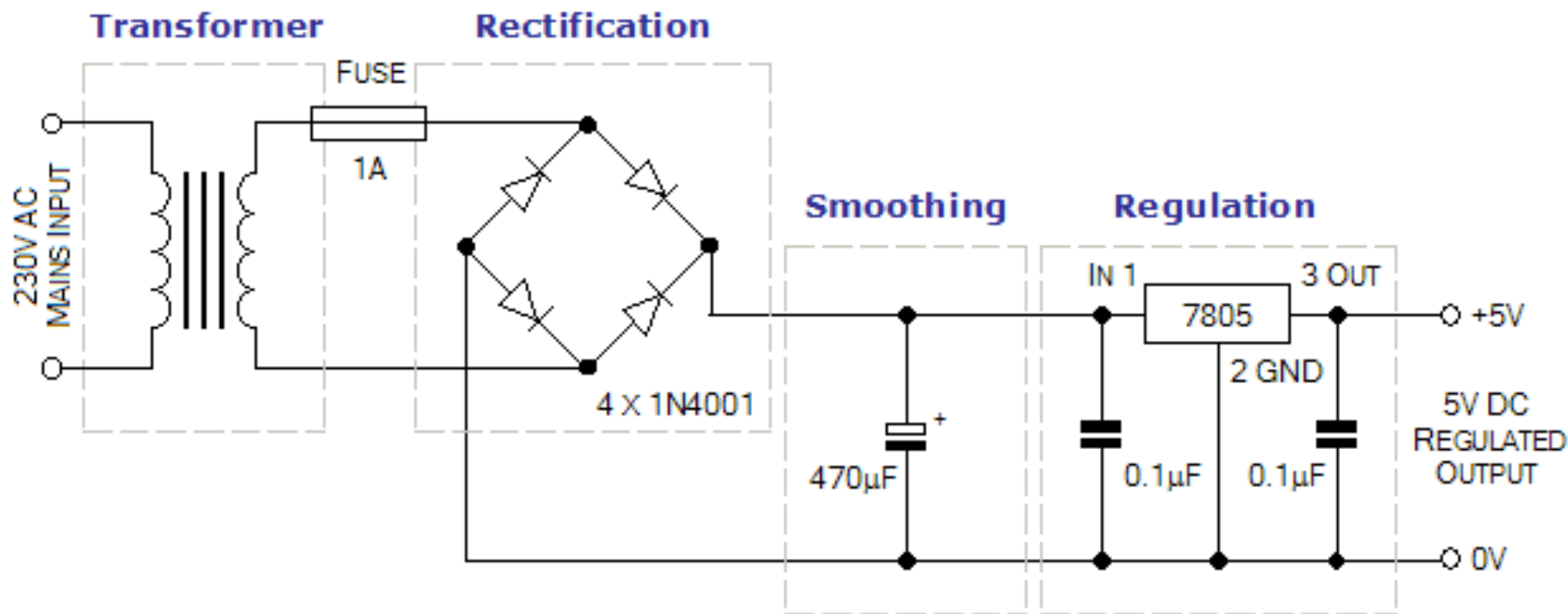

Transformer


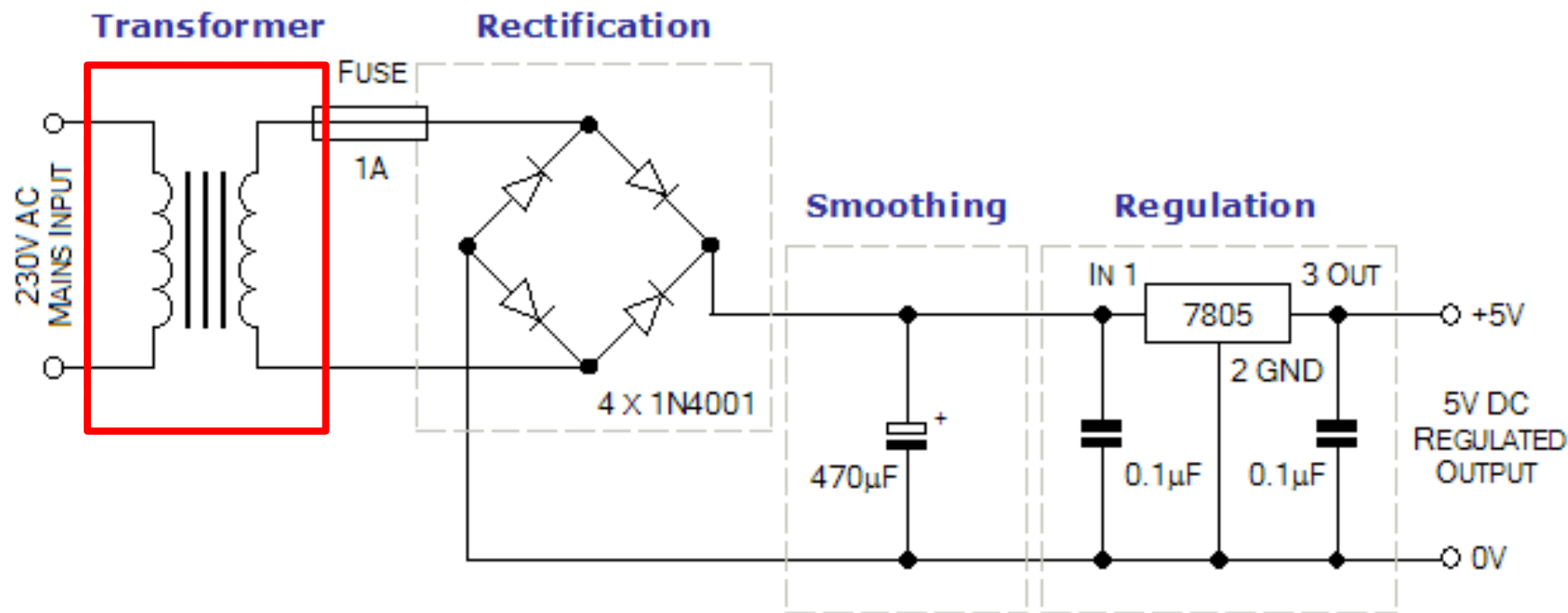


Transformer


- Step-Up Transformer
- Step-Down Transformer
 - Single-Ended
 - Centre-Tap
- Auto-Transformer

Conversion Equation:


$$\frac{V_p}{V_s} = \frac{n_p}{n_s}$$

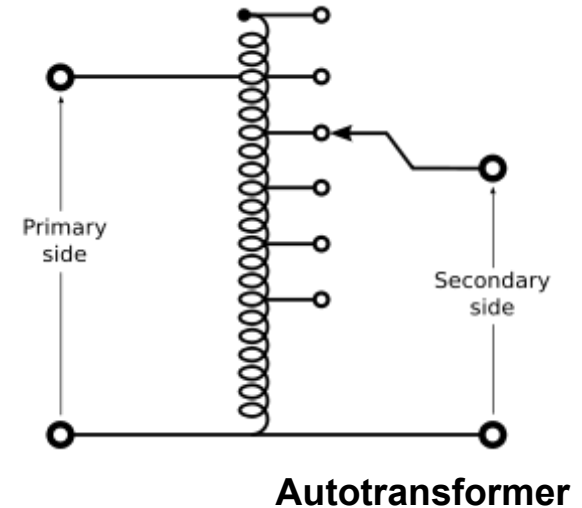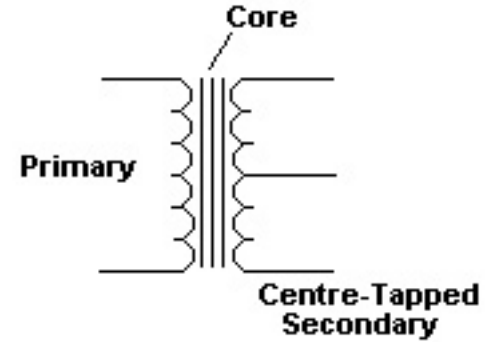

Rectifier

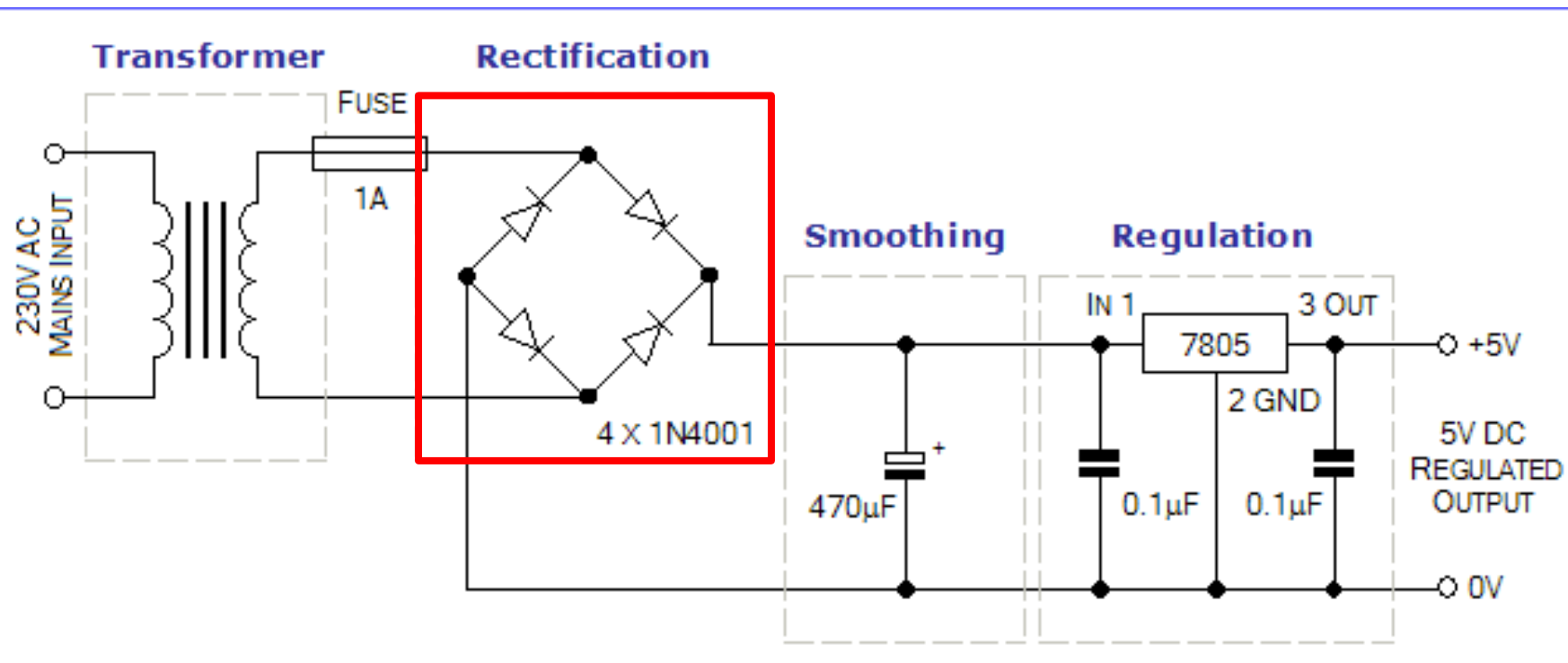


Full-Wave Rectifier

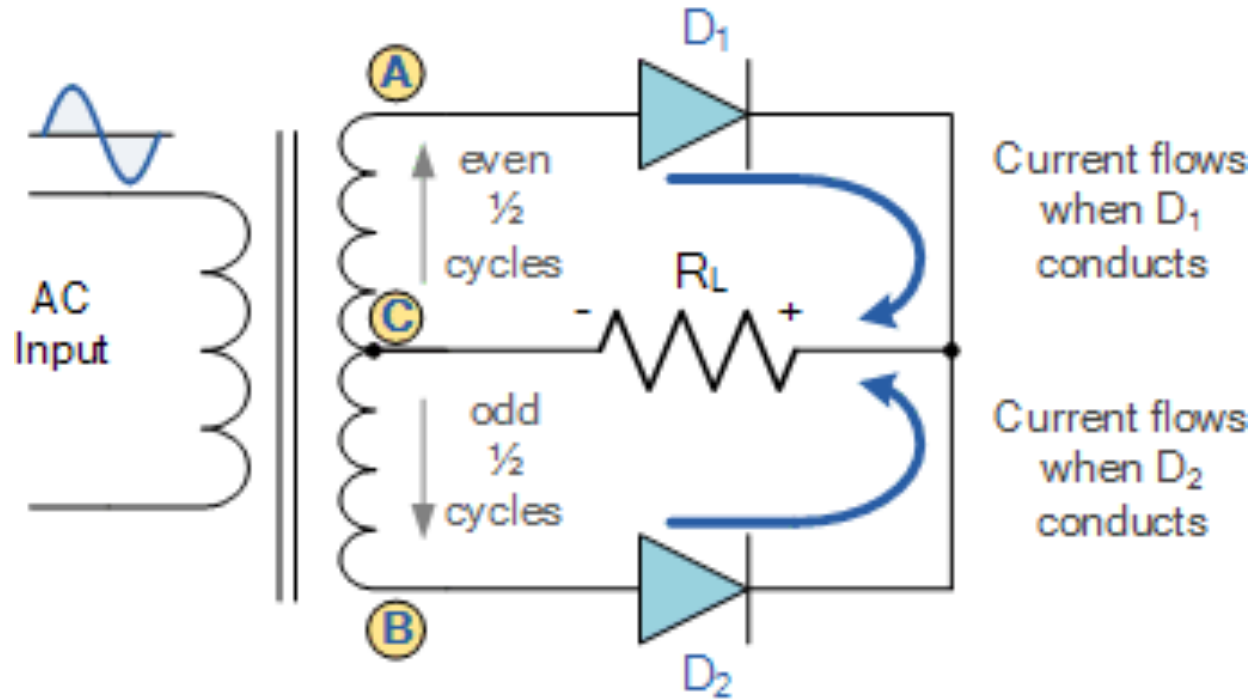

Source: http://www.electronics-tutorials.ws/diode/diode_6.html

Bridge Rectifier IC's

Various types of Bridge Rectifiers

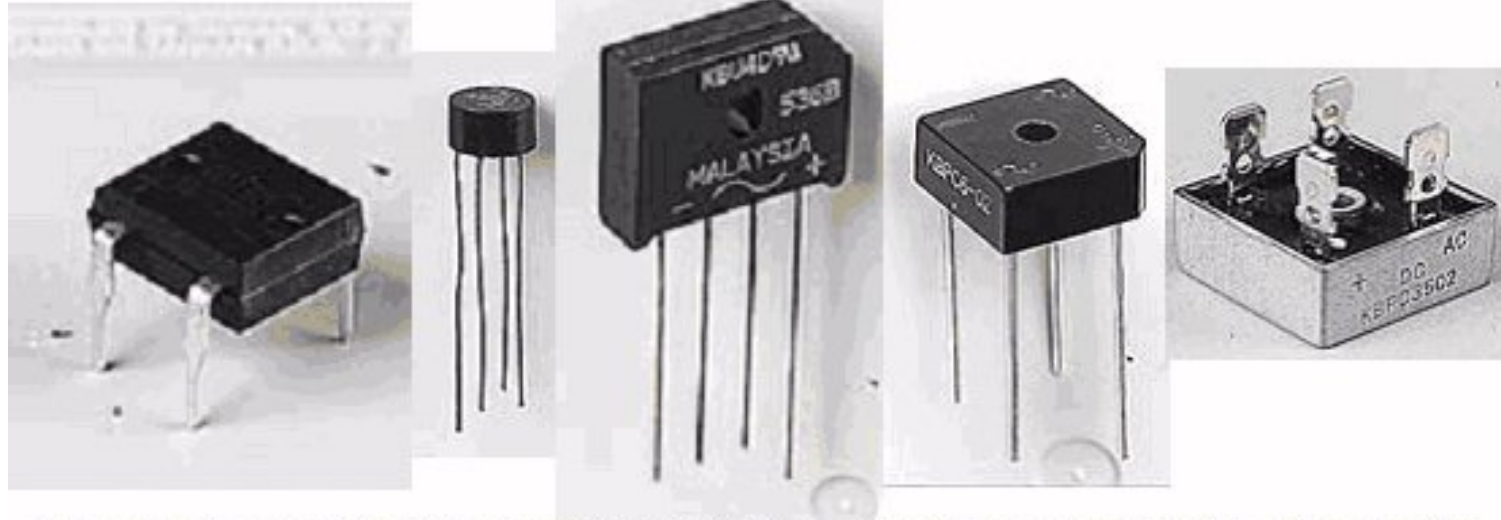


Note that some have a hole through the centre for attaching to a heat sink



Photographs courtesy of Rapid Electronics

Source: http://www.merg.org.uk/merg_resources/images/Bridge-3.jpg


Filter

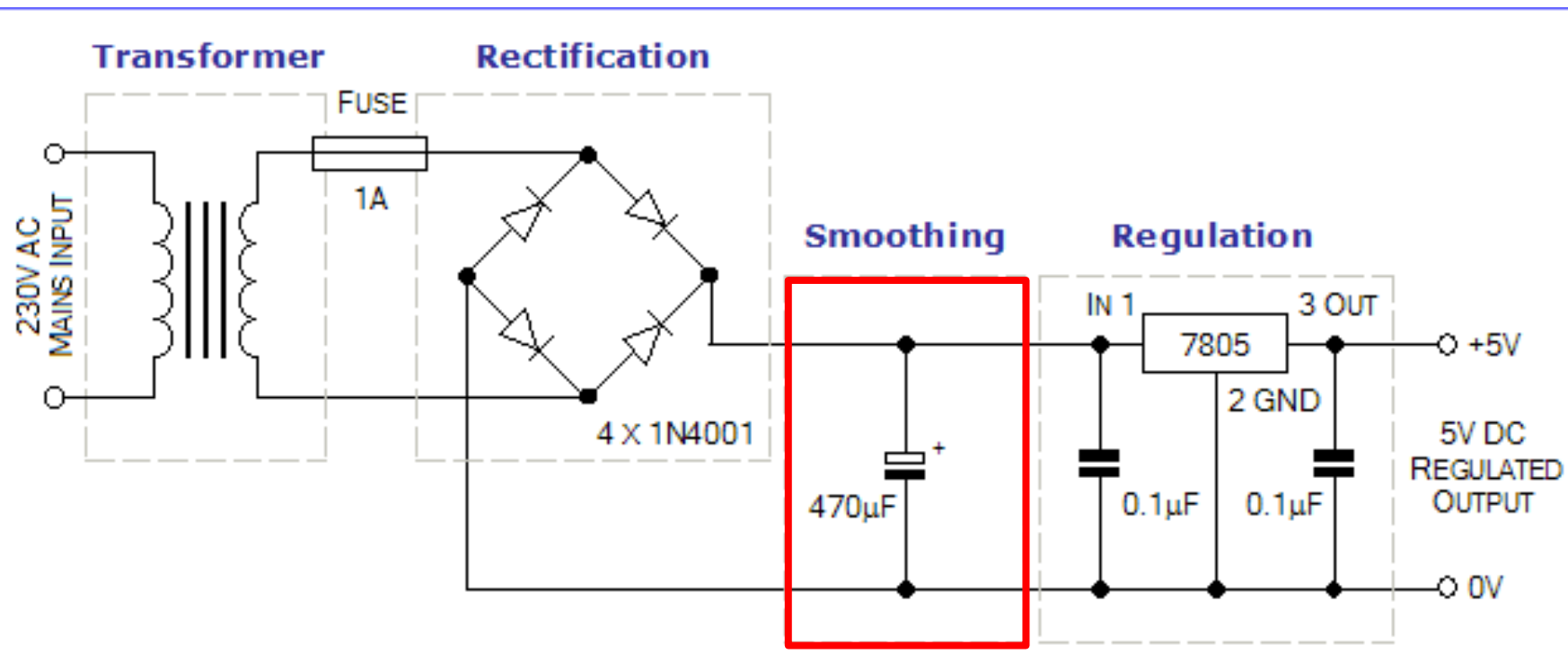


Low Pass Filter

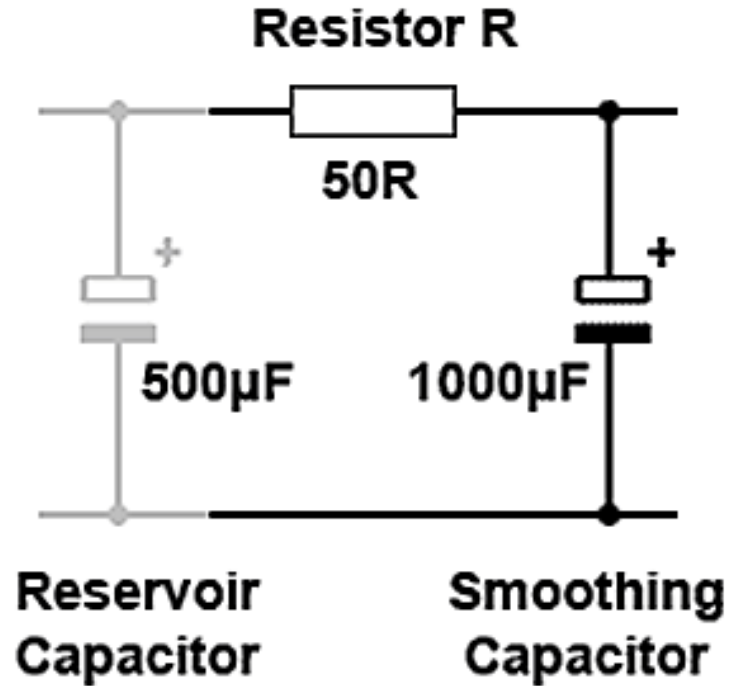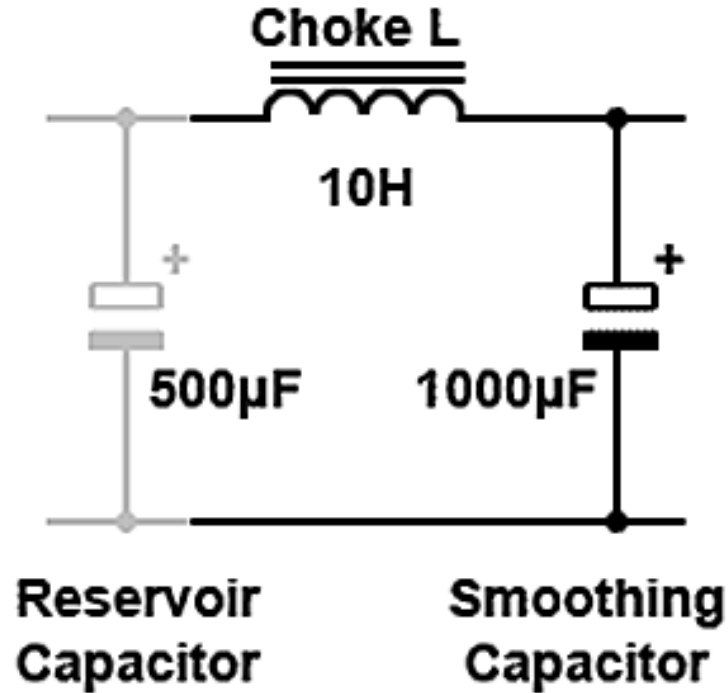

Regulator

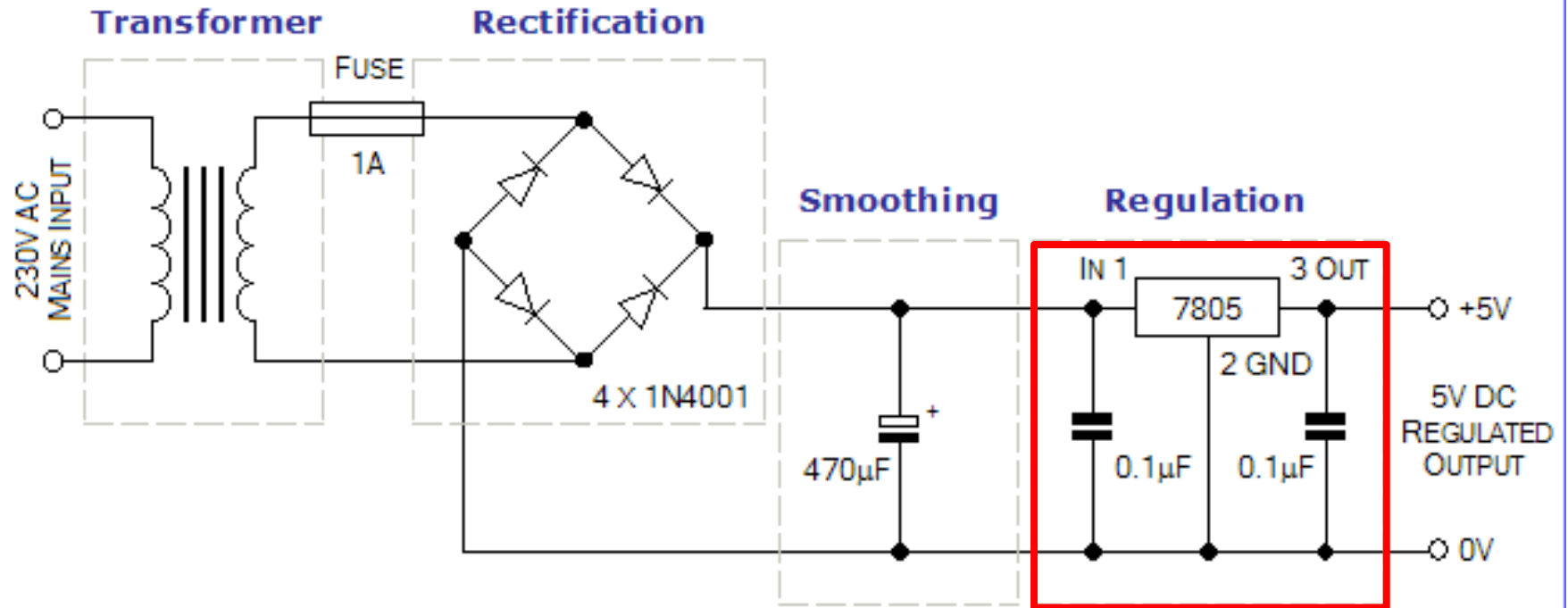


Regulator IC

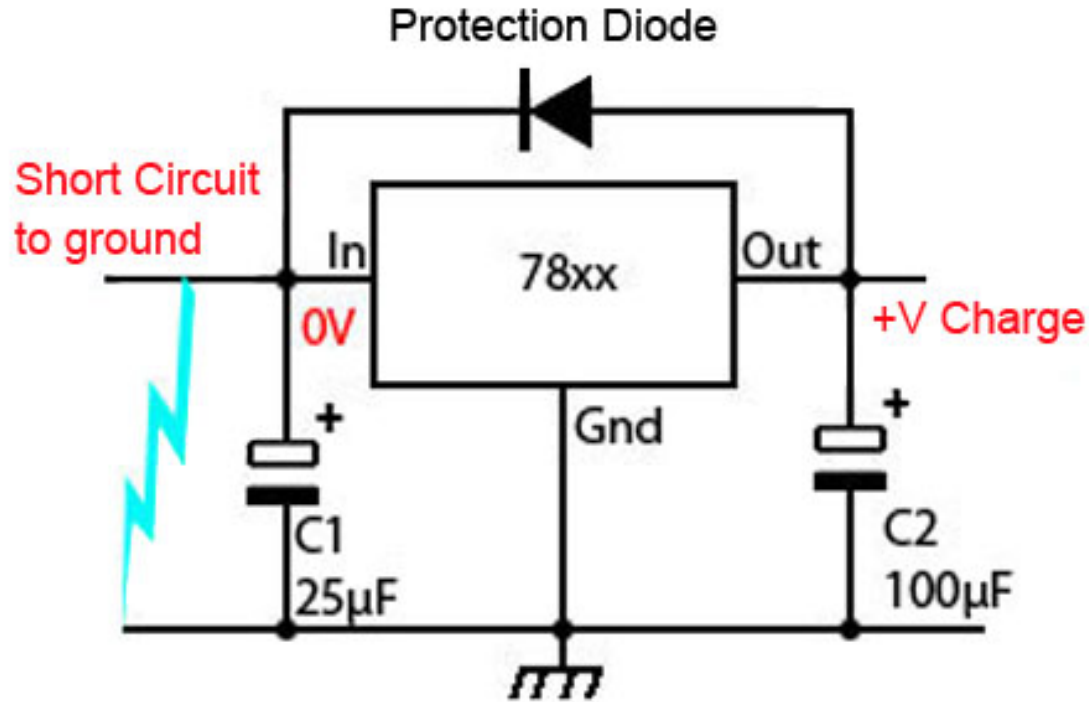

Source: <http://www.learnabout-electronics.org/PSU/images/78xx-protection-diode.jpg>

Low Dropout Regulator

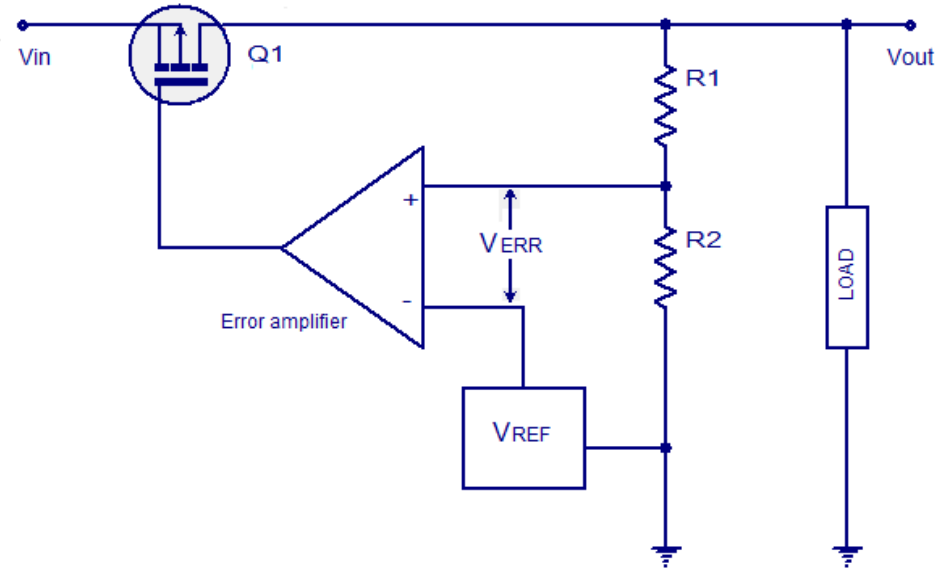
A low-dropout or **LDO** regulator is a DC linear voltage regulator which can regulate the output voltage even when the supply voltage is very close to the output voltage.



Regulated DC Power Supply

- **Transformer** - Steps-down the AC Supply
 - **Rectifier** - Produces a varying DC Supply
 - **Filter** - Filters out the variations
 - **Regulator** - Stable output.
-
- Output is constant irrespective of:
 - AC Supply
 - Load Current drawn
 - Temperature


Block Diagram

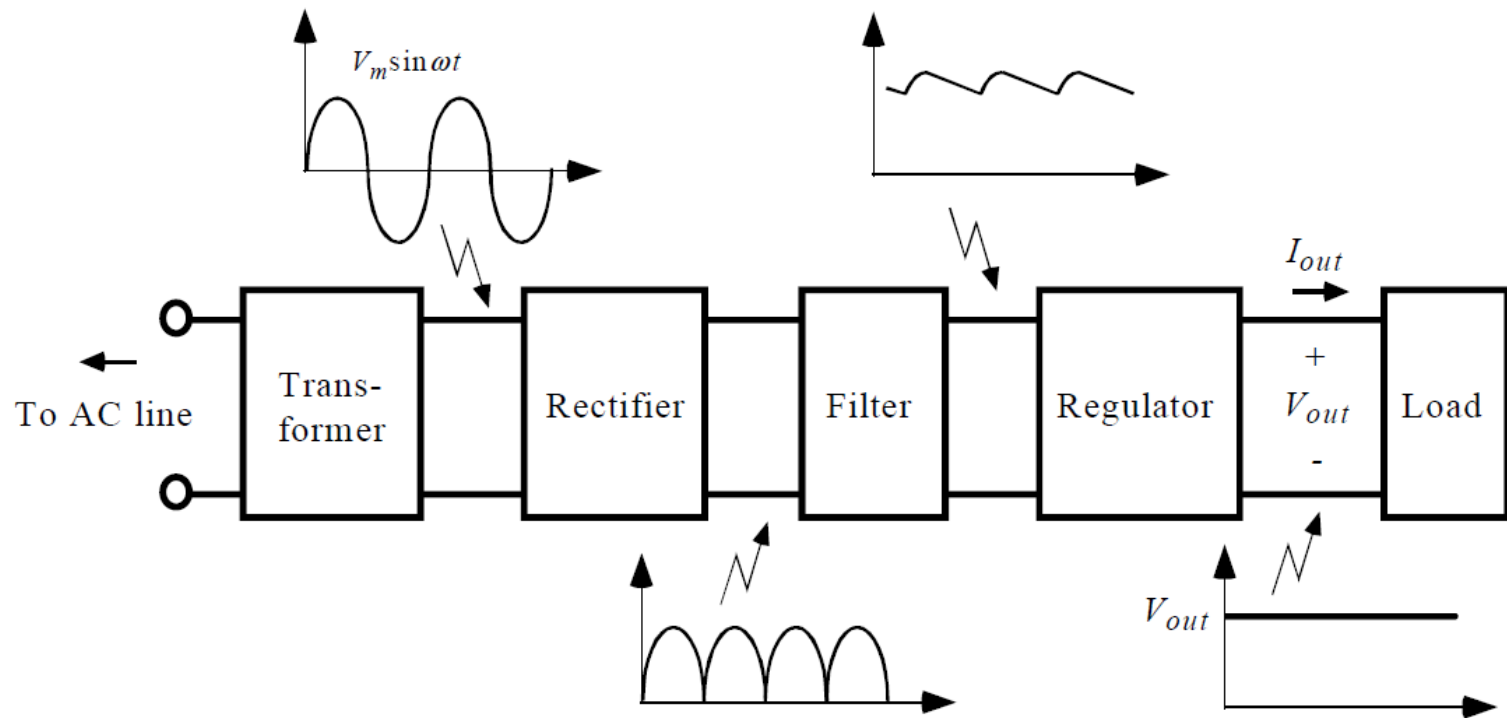

Components of a typical linear power supply

Source: <http://www.learnabout-electronics.org/PSU/psu10.php>

Switched-Mode Power Supply

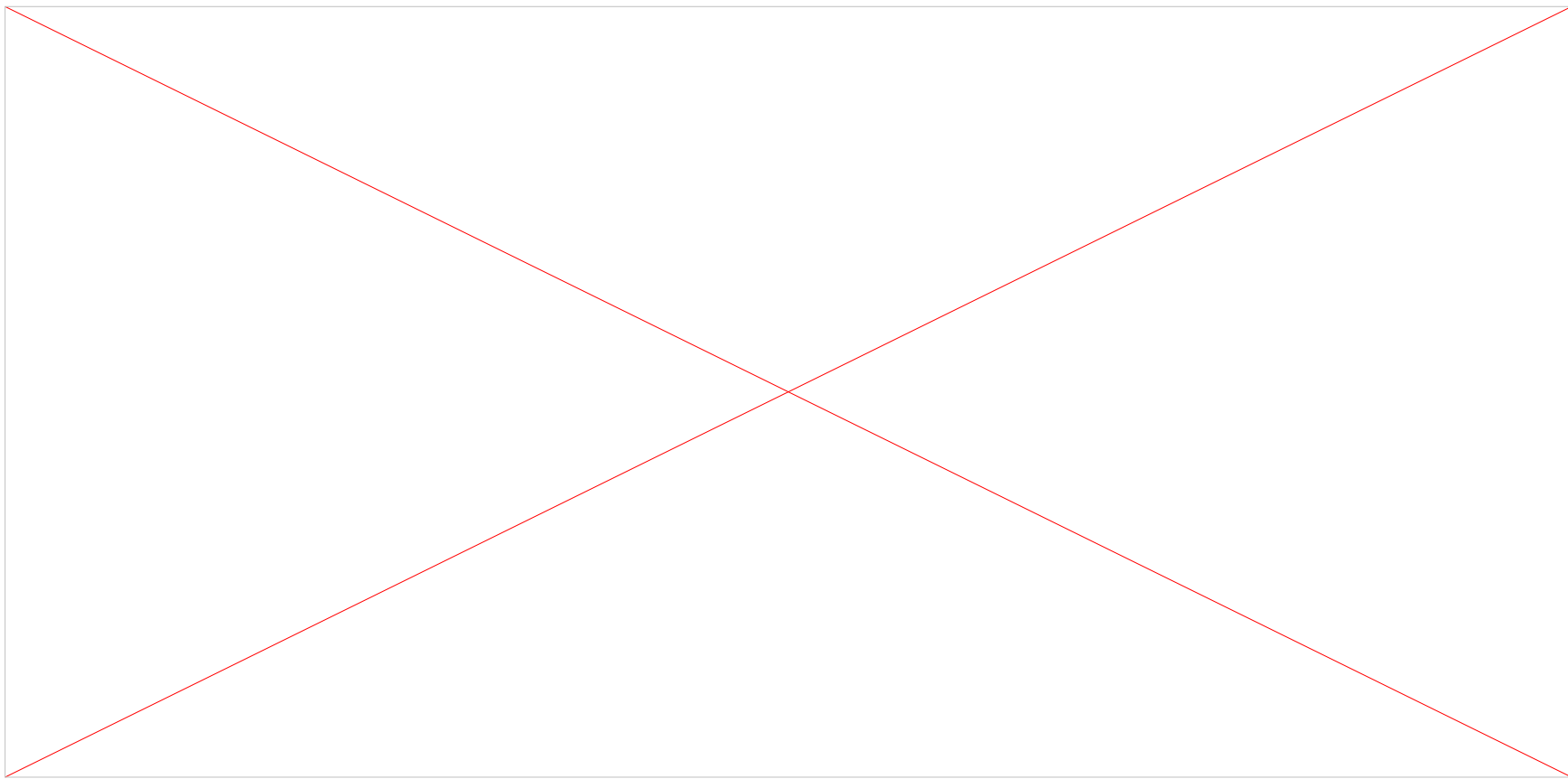


SMPS

- A switched-mode power supply is an electronic power supply that incorporates a switching regulator to convert electrical power efficiently.


Types of SMPS:

- Buck Converter (for Stepping Down)
- Boost Converter (for Stepping Up)
- Buck-Boost Converter
- Push-Pull SMPS

Buck Converter

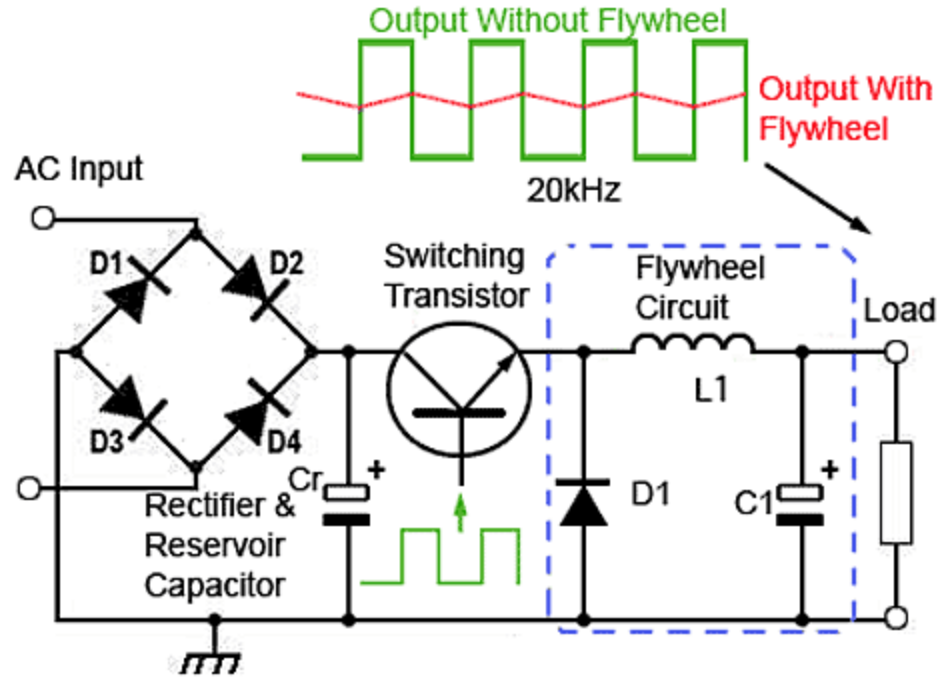

Boost Converter

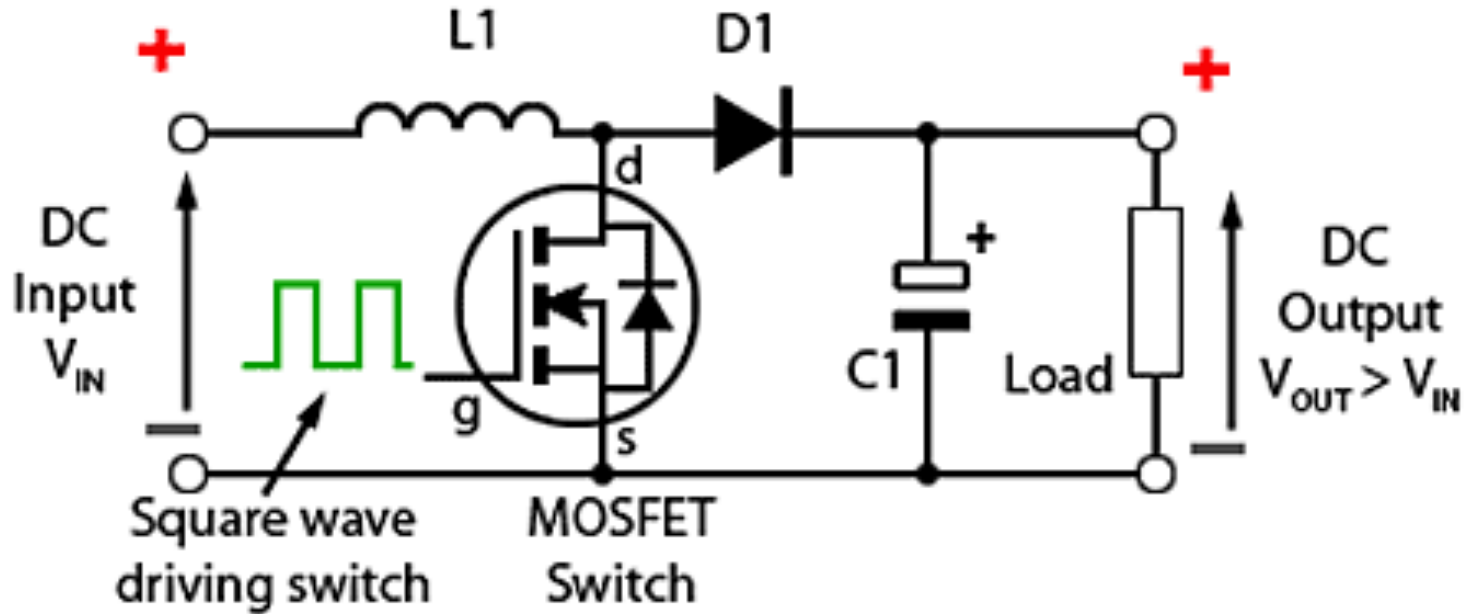

Source: <http://www.learnabout-electronics.org/PSU/images/boost-converter-basic-cct.gif>

Let's Get To The Practical